

Python Assignment No. 8

Ganga Meghanath

EE15B025

Objective :

- Symbolic Algebra
- Analysis of Circuits using Laplace Transforms

Code :

```
import sympy as sym
import pylab as p
import numpy as np
import scipy.signal as sp
import matplotlib.pyplot as mp

s=sym.symbols('s')

def lowpass(R1,R2,C1,C2,G,n,Vi) :
    A=sym.Matrix([[0,0,1,-1/n],[-1/(1+s*R2*C2),1,0,0],\
                  [0,-G,G,1],[-1/R1-1/R2-s*C1,1/R2,0,s*C1]])
    b=sym.Matrix([[0],[0],[0],[-1/R1]])
    V=A.inv()*b
    Vo=Vi*(-1)*V[3]
    return (A,b,Vo)

def highpass(R1,R3,C1,C2,G,n,Vi) :
    A=sym.Matrix([[C1*s+1/R1+C2*s,-C2*s,0,-1/R1],\
                  [-C2*s,1/R3+C2*s,0,0],[0,0,1/(n-1)+1,-1/(n-1)],[0,1,-1,1/G]])
    b=sym.Matrix([[C1*s],[0],[0],[0]])
    V=A.inv()*b
    Vo=Vi*V[0]
    return (A,b,Vo)
```

```

def impulse_response(Vo):          #Compute and plot impulse response
    w=p.logspace(0,8,801)
    ss=1j*w
    hf=sym.lambdify(s,Vo,'numpy')
    v=hf(ss)
    p.loglog(w,abs(v),lw=2)
    p.grid(True)
    p.title('Impulse Response')
    p.xlabel('w (log scale)')
    p.ylabel('log |H(jw)|')
    p.show()

def output(Vo,a,b,n):    #compute and plot time domain response
    numerator,denominator=sym.simplify(Vo).as_numer_denom()
    try :
        num,den=sym.Poly(numerator).all_coeffs(),\
            sym.Poly(denominator).all_coeffs()
    except :
        num,den=(numerator),sym.Poly(denominator).all_coeffs()
    H=sp.lti(np.array(num,float),np.array(den,float))
    t,x=sp.impulse(H,None,np.linspace(a,b,n))
    mp.plot(t,x)
    mp.title("Output")
    mp.xlabel('Time')
    mp.ylabel(r'$v_o(t)$')
    mp.show()

def damped_sine(Vo,a,w0):      #For question 4
    Vi=w0/((s+a)**2 + w0**2)
    Vo2=Vo*Vi
    output(Vo2,0,0.6,10001)

#Question 1
A,b,Vo=lowpass(1000.0,1000.0,1e-6,1e-6,1000.0,2,1)
impulse_response(Vo)
Vi=1/s
Vo=Vo*(-Vi)
output(Vo,0,0.01,1001)

#Question 2 and 3
A,b,Vo=highpass(1000.0,1000.0,1e-6,1e-6,1000.0,2,1)
impulse_response(Vo)
Vi=2000*np.pi/(s**2 + (2000*np.pi)**2) + s/(s**2 + (2e6*np.pi)**2)
Vo1=Vo*Vi
output(Vo1,0,0.01,100001)
output(Vo1,0,0.00009,10001)

```

```

#Question 4
damped_sine(Vo,10,800)
damped_sine(Vo,20,500)

#Question 5
Vi=1/s
Vo3=Vo*Vi
output(Vo3,0,0.05,1001)

```

Question 1

```

def lowpass(R1,R2,C1,C2,G,n,Vi) :
    A=sym.Matrix([[0,0,1,-1/n],[-1/(1+s*R2*C2),1,0,0],\
                  [0,-G,G,1],[-1/R1-1/R2-s*C1,1/R2,0,s*C1]])
    b=sym.Matrix([[0],[0],[0],[-1/R1]])
    V=A.inv()*b
    Vo=Vi*(-1)*V[3]
    return (A,b,Vo)

def impulse_response(Vo):          #Compute and plot impulse response
    w=p.logspace(0,8,801)
    ss=1j*w
    hf=sym.lambdify(s,Vo,'numpy')
    v=hf(ss)
    p.loglog(w,abs(v),lw=2)
    p.grid(True)
    p.title('Impulse Response')
    p.xlabel('w (log scale)')
    p.ylabel('log |H(jw)|')
    p.show()

def output(Vo,a,b,n):             #compute and plot time domain response
    numerator,denominator=sym.simplify(Vo).as_numer_denom()
    try :
        num,den=sym.Poly(numerator).all_coeffs(),sym.Poly(denominator)
    except :
        num,den=(numerator),sym.Poly(denominator).all_coeffs()
    H=sp.lti(np.array(num,float),np.array(den,float))
    t,x=sp.impulse(H,None,np.linspace(a,b,n))
    mp.plot(t,x)
    mp.title("Output")
    mp.xlabel('Time')


```

```
mp.ylabel(r'$v_o(t)$')
mp.show()
```
 
#Question 1


```
A,b,Vo=lowpass(1000.0,1000.0,1e-6,1e-6,1000.0,2,1)
impulse_response(Vo)
Vi=1/s
Vo=Vo*(-Vi)
output(Vo,0,0.01,1001)
```

This gives us a low pass filter. This means that all signal frequencies below the filter bandwidth will be allowed to pass through the filter.



Step response of the filter ,
ie, Output of the highpass filter when the input is :

$$v_i(t) = u_0(t)$$

 

Question 2 and 3

```
def highpass(R1,R3,C1,C2,G,n,Vi) :
    A=sym.Matrix ([[ C1*s+1/R1+C2*s,-C2*s,0,-1/R1],\
                    [-C2*s,1/R3+C2*s,0,0],[0,0,1/(n-1)+1,-1/(n-1)],[0,1,-1,1/G]])
    b=sym.Matrix ([[ C1*s], [0],[0],[0]])
    V=A.inv()*b
    Vo=Vi*V[0]
    return (A,b,Vo)

def impulse_response(Vo):          #Compute and plot impulse response
    w=p.logspace(0,8,801)
    ss=1j*w
    hf=sym.lambdify(s,Vo,'numpy')
    v=hf(ss)
    p.loglog(w,abs(v),lw=2)
    p.grid(True)
    p.title('Impulse Response')
    p.xlabel('w (log scale)')
    p.ylabel('log |H(jw)|')
    p.show()

def output(Vo,a,b,n):             #compute and plot time domain response
    numerator,denominator=sym.simplify(Vo).as_numer_denom()
```

```

try :
    num,den=sym.Poly(numerator).all_coeffs(),sym.Poly(denominator)
except :
    num,den=(numerator),sym.Poly(denominator).all_coeffs()
H=sp.lti(np.array(num,float),np.array(den,float))
t,x=sp.impz(H,None,np.linspace(a,b,n))
mp.plot(t,x)
mp.title("Output")
mp.xlabel('Time')
mp.ylabel(r'$v_o(t)$')
mp.show()

```

#Question 2 and 3

```
A,b,Vo=highpass(1000.0,1000.0,1e-6,1e-6,1000.0,2,1)
```

```
impz_response(Vo)
```


```
Vi=2000*np.pi/(s**2 + (2000*np.pi)**2) + s/(s**2 + (2e6*np.pi)**2)
```

```
Vol=Vo*Vi
```

```
output(Vol,0,0.01,100001)
```


```
output(Vol,0,0.00009,10001)
```

 This gives us a high pass filter. This means that all signal frequencies above the filter bandwidth will be allowed to pass through the filter.




Output of the filter when the input is :
 
$$v_i(t) = (\sin(2000\pi t) + \cos(2 \times 106\pi t)) * u_0(t)$$



Zooming in :

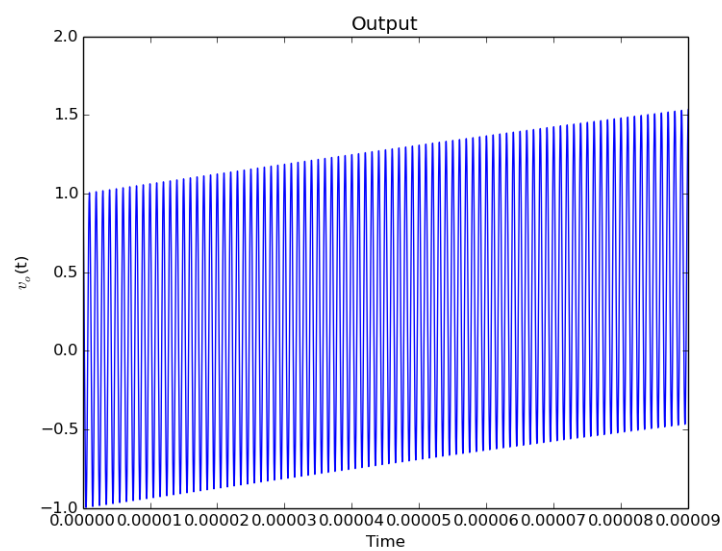

Question 4

```
def output(Vo,a,b,n):    #compute and plot time domain response
    numerator,denominator=sym.simplify(Vo).as_numer_denom()
```

```

try :
    num,den=sym.Poly(numerator).all_coeffs(),sym.Poly(denominator)
except :
    num,den=(numerator),sym.Poly(denominator).all_coeffs()
H=sp.lti(np.array(num,float),np.array(den,float))
t,x=sp.impulse(H,None,np.linspace(a,b,n))
mp.plot(t,x)
mp.title("Output")
mp.xlabel('Time')
mp.ylabel(r'$v_o(t)$')
mp.show()


def damped_sine(Vo,a,w0): #For question 4
    Vi=w0/((s+a)**2 + w0**2)
    Vo2=Vo*Vi
    output(Vo2,0,0.6,10001)

#Question 4
damped_sine(Vo,10,800)
damped_sine(Vo,20,500)

```


Output of the high pass filter when the input is :

$$v_i(t) = e^{-10t} \sin(800t)$$

 

Output of the highpass filter when the input is :

$$v_i(t) = e^{-20t} \sin(500t) * u_0(t)$$

 

Question 5

```
def output(Vo,a,b,n):    #compute and plot time domain response
    numerator,denominator=sym.simplify(Vo).as_numer_denom()
    try :
        num,den=sym.Poly(numerator).all_coeffs(),sym.Poly(denominator)
    except :
        num,den=(numerator),sym.Poly(denominator).all_coeffs()
    H=sp.lti(np.array(num,float),np.array(den,float))
    t,x=sp.impulse(H,None,np.linspace(a,b,n))
    mp.plot(t,x)
    mp.title("Output")
    mp.xlabel('Time')
    mp.ylabel(r'$v_o(t)$')
    mp.show()
```

```
#Question 5
Vi=1/s
Vo3=Vo*Vi
output(Vo3,0,0.05,1001)
```

Output of the highpass filter when the input is :

$$v_i(t) = u(t)$$

